

Voltage, Current, Resistance, Capacitance, Power

$$V = IR$$

$$P = IV$$

$$P = I^2R$$

$$Q = CV$$

$$P = \frac{V^2}{R}$$

$$kWh = (kW)(hr)$$

V - Voltage; *I* - Current, *C*; *R* - Resistance, Ω ; *C* - Capacitance, *F*; *P* - Power, *W*; *E* - Energy, *J*; *kWh* - Kilowatt-Hours

Energy and Work

$$E = Pt$$

$$E = IVt$$

$$W = Vq$$

E - Energy, *J*; *P* - Power, *W*; *t* - time, *s*; *I* - Current, *A*;
V - Voltage; *P* - Power, *W*; *W* - Work, *J*; *q* - Charge, *C*;

Quantity of Charge

$$n = It$$

n - Number of charges; *I* - Current, *A*; *t* - time, *s*

Amps, Coulombs, Electrons

1 Ampere = 1 Coulomb / second

1 Coulomb = 6.242×10^{18} electrons

Series and Parallel Circuits

Series Circuits



$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

- ▷ Current is the same through all resistors
- ▷ Voltage may be different across each resistor
- ▷ Individual voltages add up to the total voltage at the source

Parallel Circuits



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

- ▷ Voltage is the same across all resistors
- ▷ Current may be different through each resistor
- ▷ Individual currents add up to the total current at the source